

DIYPowerPCB

Introduction


Theoretical derivations in a lecture are part of everyday university life. But you can only really get to grips with topics if you apply what you have learned! For this reason, we have developed the DIY Power PCB. This enables us to provide all interested students with their own hardware platform to carry out a wide variety of experiments on the subject of power electronics.

The idea was not to build the most powerful or the smallest hardware, but a hardware whose components can largely be assembled automatically and which is above all inexpensive and robust. So no worries if a short circuit is generated or



smoke rises

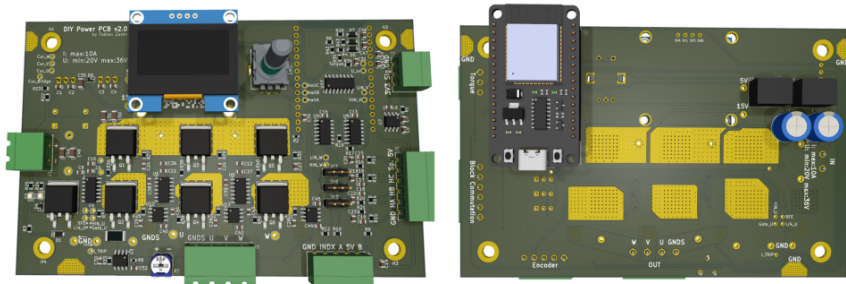The DIY Power PCB is used in various experiments in the lectures on power electronics and electrical drives and costs less than 20€ for our students when fully assembled.



Parameters:

- 3x half bridges
- Adjustable overcurrent shutdown
- ESP32 Wroom microcontroller
- 1.36 OLED display
- Max. 36V @10A input
- Hall sensor or encoder inputs
- General purpose analog input

- Reverse polarity protection

The brain of the board is represented by an ESP32 microcontroller. This controller is very powerful and widely available at affordable prices. You can directly program it using the Arduino IDE or ESP-IDF. For lab lessons, you will use a serial communication interface between MATLAB Simulink and the controller to command the board.

[Schematic:](#)

schematic_diy_power_pcb.pdf

To use the DIY Power PCB, you can program the ESP32 using the Arduino IDE or the ESPRESSIFWorkspace (Espressif-IDE) development platform. Arduino IDE is more intuitive; however, it is not capable of utilizing the full range of the timer units. Espressif-IDE allows you to access the full functionality of the microcontroller, and the programmer is also faster than the Arduino IDE. However, it is more complicated to get started with.

Board Flyer




H
T
W
G
I

DIY POWER PCB

Multi Purpose Power Electronic Board

Hochschule Konstanz
Fakultät Elektrotechnik
und Informationstechnik

The DIY Power PCB can be used to build a wide variety of basic power electronics circuits. A simple buck converter can be set up with each of the three phases opposite the GNDs potential. If two phases are used, an inverter can be built with synchronous clocking or as a phase shifted full bridge. All three half bridges U, V, W can be used to control a BLDC motor and a synchronous machine or to generate a three-phase AC voltage in general.

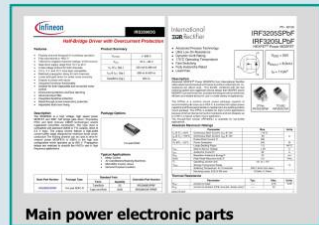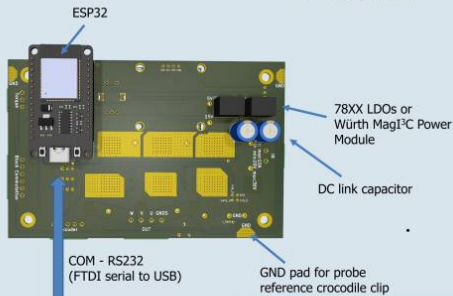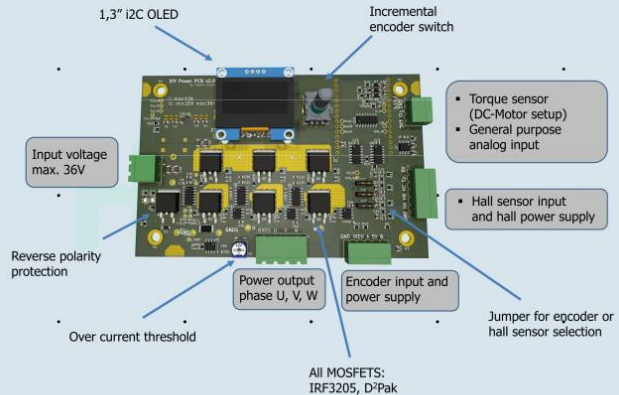

Control options

Matlab, Arduino, ESPRESSIFWORKSPACE

To use the DIY Power PCB, you can program the ESP32 using the Arduino IDE or the ESPRESSIFWORKSPACE (Espressif-IDE) development platform. Arduino IDE is more intuitive, however, it is not capable of utilizing the full range of the timer units. Espressif-IDE allows you to access the full functionality of the microcontroller, the programmer is also faster than the Arduino IDE. However, it is more complicated to get started with.

MinebeaMitsumi BLDC Motor



Accessories

Dunkermotoren Brushed DC Motor GR 63x55



Würth Electronic Inductor / Capacitor



Prof. Dr.-Ing. Heinz Rebholz – HTWG Konstanz – heinz.rebholz@htwg-konstanz.de

Additional features:

- Maximum input current of 10A
- Optional ACS712_XX current sensors for every half bridge
- Adjustable over current threshold
- ESP32 with WiFi and Bluetooth connection



Downloads

Version 2.3

Version 2.3 of DIY Power PCB KiCAD Files:

Version 2.2

Version 2.2 of DIY Power PCB KiCAD Files:

Download

General Information

If you want to generate fancy 3D images you have to download the model files:

Download 3D Models

The content of the .zip must be saved in the "3dmodels" folder of KiCAD in a new folder with the name "htwg.3dshapes".

If your PC does not recognize a USB-to-serial connection, you might not have installed the correct driver yet: Download the latest drivers: [Link to FTDI](#)

Isolation

In many of our experiments, we control the hardware via the serial interface. To protect the connected PC, you should use galvanic isolation between the PC and the microcontroller board when the supply voltage is active. This prevents overvoltages from destroying the USB port even in the event of major errors in the setup (short circuit or load dump) on the control PC.

The isolators are available in the laboratory.

z.B.





4,99€ ca. 54% günstiger

Neuer Preis

100% Versand und Rückversandgarantie erhöht

ESD inklusive 150000 Isolierstich-APR, PROSAFE Produkt-Prüfung 30-Tage-Bond, ESD bis 1500 inklusive mit USB 3.0

★★★★★ 4,3 (20 Bewertungen) · 238 verkauft

Einen Filter mit 3-Wege



Weitere Produktinformationen 

Verkaufsort: Simple Robot Store (Händler)

Lieferumfang: 1x USB Dongle, Bedienungsanleitung...

Abgabeverpflichtung:

- ☒ Versand 2.50€ (Lieferung: 02.08 - 03)
- ☐ Abgabe bis 10 Tage voran
- ☐ Rückgabe und Garantie (siehe Angaben Produktbeschreibung)

Frage:

☐ & ☐ 100% erfüllt

Jetzt kaufen

In den Warenkorb

  262

Kundenbewertungen (20) [Spezialaktionen](#) [Über mich](#) [Laden](#) [Die kleine Site aus Konstanzen](#)